

### Logic Gate 3 : NOT, AND, OR gates

