

## Logic Gate 2: 4:16 "one-hot" decoder & OR gates

